

UNIVERSITY OF SUSSEX  
Scientific Computing  
Tutor: Dr. Ilian Iliev, Office: Pev 3 4C5

**Problem Sheet 1 (Problem 2 will be assessed)**


**Deadline: 12pm on Monday, October 31st, 2016.**

Penalties will be imposed for submissions beyond this date.

**Final submission date: Tuesday, November 1st, 2016.**

**No submissions will be accepted beyond this date.**

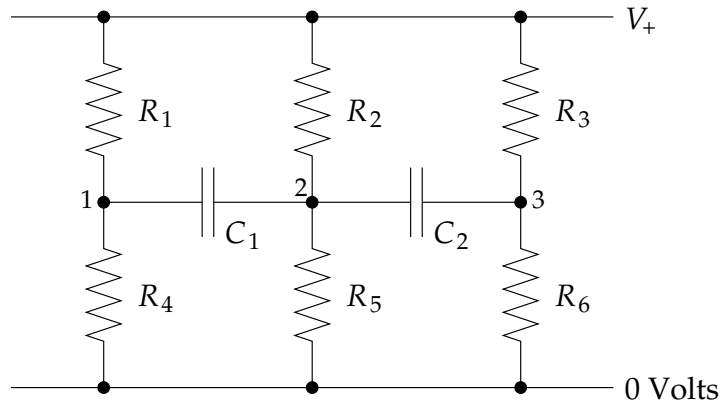1. Use the built-in NumPy function `random.random` to create the  $n \times n$  random matrix  $A$ , in which all elements have values between 0 and 10.
  - (a) Use this to create an  $n \times n$  matrix  $A$  for  $n=50, 100, 200, 300$ , and  $400$  using a for loop.
  - (b) For this matrix  $A$  construct a vector  $b$  so that the solution to  $Ax = b$  is  $x = [1, 2, \dots, n]$ .
  - (c) Test your construction by applying Gauss elimination to compute  $x$ . What is the largest element-by-element error for each  $n$ ? Plot the decimal log of the max element-by-element error vs.  $n$ . Comment on the results.
2. **(Assessed)** Consider the following RC circuit:



The voltage  $V_+$  is time-varying and sinusoidal of the form  $V_+ = x_+ e^{i\omega t}$  with  $x_+$  a constant. The resistors in the circuit can be treated using Ohm's law as usual. For the capacitors the charge  $Q$  and voltage  $V$  across them are related by the capacitor law  $Q = CV$ , where  $C$  is the capacitance. Differentiating both sides of this expression gives the current  $I$  flowing in on one side of the capacitor and out on the other:

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}.$$

- (a) Assuming the voltages at the points labeled 1, 2, and 3 are of the form  $V_1 = x_1 e^{i\omega t}$ ,  $V_2 = x_2 e^{i\omega t}$ , and  $V_3 = x_3 e^{i\omega t}$ , apply Kirchhoff's law at each of the three points, along with Ohm's law and

the capacitor law, to show that the constants  $x_1$ ,  $x_2$ , and  $x_3$  satisfy the equations

$$\begin{aligned}\left(\frac{1}{R_1} + \frac{1}{R_4} + i\omega C_1\right)x_1 - i\omega C_1 x_2 &= \frac{x_+}{R_1}, \\ -i\omega C_1 x_1 + \left(\frac{1}{R_2} + \frac{1}{R_5} + i\omega C_1 + i\omega C_2\right)x_2 - i\omega C_2 x_3 &= \frac{x_+}{R_2}, \\ -i\omega C_2 x_2 + \left(\frac{1}{R_3} + \frac{1}{R_6} + i\omega C_2\right)x_3 &= \frac{x_+}{R_3}.\end{aligned}$$

(b) Write a program to solve for  $x_1$ ,  $x_2$ , and  $x_3$  when

$$\begin{aligned}R_1 &= R_3 = R_5 = 1 \text{ k}\Omega, \\ R_2 &= R_4 = R_6 = 2 \text{ k}\Omega, \\ C_1 &= 1 \mu\text{F}, \quad C_2 = 0.5 \mu\text{F}, \\ x_+ &= 3 \text{ V}, \quad \omega = 1000 \text{ s}^{-1}.\end{aligned}$$

Notice that the matrix for this problem has complex elements. You will need to define a complex array to hold it, but you can still use the `solve` function just as before to solve the equations—it works with either real or complex arguments. Using your solution have your program calculate and print the amplitudes of the three voltages  $V_1$ ,  $V_2$ , and  $V_3$  and their phases in degrees. (Hint: You may find the functions `polar` or `phase` in the `cmath` package useful. If  $z$  is a complex number then “`r, theta = polar(z)`” will return the modulus and phase (in radians) of  $z$  and “`theta = phase(z)`” will return the phase alone.)

[40]